

# EE620 — Project1 Assignment Design of Digital systems

**From:** DINESH ANAND BASHKARAN

**UID:** 570000943

**Date Due:** 09/26/2016.

## INTRODUCTION:

This project is all about CMOS design for various combinations of basic gates. Design of inverter, NAND, NOR, XOR, 2input OAI (OR-AND-INVERTER) and Transmission 2:1 multiplexer is designed in this project. This is done using a 45nm CMOS technology in the cadence virtuoso. The software provides an excellent base to test the design in user defined way considering the rules that has to be followed for ideal design. The ultimate aim of the project is to provide knowledge regarding the issues faced in designing a CMOS circuit with respect to various factors from start of design until the desired output is reached. The technology used is 45nm which provides the limitation to size of transistors that apparently leads to scaling them down. Once the layout is designed, the variation in rise/fall time can be computed which

directly shows how fast the design was made. It also gives a chance to compare the switching time for different combination of circuits.

### **Discussions:**

The specified base reference size for NMOS is  $12\lambda/2\lambda$  which sets the size as 270nm/45nm and for PMOS is x2 size of NMOS which ends in 540nm/45nm. The technology used is 45nm, fingers are used to break down the size and construct multiple transistors to have an equivalent specification. In order to maintain the equivalent resistance across the PMOS and NMOS the width is adjusted respectively. The mobility in PMOS/NMOS is constant but the resistance in PMOS is twice that of NMOS, in order to maintain equal charging and discharging the resistance has to be maintained at "R", for which the width of the transistor are adjusted accordingly. Generally, wider transistors have more resistance. This gives a chance to view the behavior of transistor when we change the width. When the width is increased the current and gate capacitance increases respectively.

The design of CMOS for various combination of basic gate using a 45nm technology is little bit challenging. As a matter of fact, design is always made with an idea to have least possible size after considering all the restrictions that serves for basic rule check to avoid shorting of contacts between the different layers of CMOS. The quality of design can be recognized when it comes to rise/fall time, which is computed for every single combination in this project.

Rise time here is considered as the time for the waveform to rise from 20% to 80% of the steady state value. Fall time is considered as the time for the waveform to fall from 80% to 20% of the value. Depending on how much the transistor takes to switch between ON/OFF is directly computed in the waveform. The average delay can be computed from rise and fall time.

Propagation delay is the maximum taken for the waveform to reach from the previous input to 50% of the next output which is  $V_{DD}/2$ . The average propagation delay is calculated by taking the average of worst case  $T_{pdf}$  and  $T_{pdr}$

$T_{pdf}$ = propagation delay falling,  $T_{pdr}$ = propagation delay rising

Average propagation delay  $T_{pd} = (T_{pdf} + T_{pdr})/2$

### **CMOS INVERTERX2:**

Equation:  $Y=A'$

The design of inverter is done with the size of NMOS as 540nm/45nm and to PMOS is 1080nm/45nm. The technology has a restriction to size which leads to usage of fingers with multiple transistors in parallel. Since, the resistance of PMOS is twice that of NMOS the width is adjusted respectively to maintain the charge and discharge. The design is made to utilize minimum size as possible. The propagation delay for falling and rising is also calculated  $T_{pdr}$  is 310.8ns and  $T_{pdf}$  is 354ns. This is computed on the layout considering all the parasitic values which has impact on the output values.

Rise time with parasitic is 310.8ps

Fall time with parasitic is 354.6ps

Average propagation delay = 332.4ps

### **CMOS NAND:**

Equation:  $Y= \sim(A+B)$

The design of NAND using CMOS is done with size of NMOS as 540nm/45nm and of PMOS as 540nm/45nm. The resistance is added in series NMOS, in order to reduce the added resistance the width is doubled. Width is inversely proportional to the resistance. The design is simple and not much complication is found. Considering the propagation delay, it is calculated for single input keeping other input constant to observe the variation of output and vice versa.

Rise time with parasitic: 562.2ps

Fall time with parasitic: 709.3ps

Average propagation delay: 491.7ps

### **CMOS NOR:**

Equation:  $Y= \sim(A.B)$

The design of NOR is done with the size of NMOS as 270nm/45nm and PMOS as 1080nm/45nm. The PMOS is in series where the resistance is added, to reduce the added resistance the width of the

transistor is doubled to 1080nm/45nm. This design can be done in 3 fingers of 360nm/45nm each for PMOS. Yet, the design seems to be pretty simple and does not get complicated. The rise time is 624.1ns and fall time is 373.3ns. The propagation delay is calculated for single input and compared.

Rise time with parasitic: 624.1ps

Fall time with parasitic: 373.3ps

Average propagation delay: 523.4ps

### **CMOS OAI:**

Equation:  $Y = \sim((A0+B0).(A1+B1))$

The design of OR-AND-INVERTER with 2 inputs seems to have added series resistance in PMOS and NMOS. To maintain the equivalent resistance across PMOS and NMOS the width is doubled for both of them. PMOS of 1080nm/45nm and NMOS of 540nm/45nm is the size. The design gets little bit complicated here yet, gives the knowledge of designing 2 input combinations using CMOS. The rise time considering parasitic is 563.6ns and fall time is 406.1ns. The propagation delay is computed for every single input keeping others constant to figure the variation of output.

Rise time with parasitic: 563.6ps

Fall time with parasitic: 406.1ps

Average propagation delay: 547.6ps

### **CMOS XOR:**

Equation:  $Y = (AB' + A'B)$

The design of XOR shows up with 2 inputs which require inverted function of each other. The size of the PMOS and NMOS is doubled to maintain the equivalent resistance across them. PMOS of 1080nm/45nm and NMOS of 540nm/45nm is the size of this design. The design gets little complicated, when it comes to design of 2 base inverter with the design of XOR in single cell. The connection between different layers plays a hard role which also gives the knowledge of designing complicated circuit. The difficulty faced in this design was shorting the PMOS and NMOS with metal layer. Since metal layer needs 6λ width and 6λ spacing between them, there was not much spacing in the vertical area. Placing the Metal

on top of PMOS showed up some spacing. The rise time with parasitic is 619ns and fall time is 666.7ns. The propagation delay is calculated for every single input to find the behavior of output respectively.

Rise time with parasitic: 619ps

Fall time with parasitic: 666.7ps

Average propagation delay: 542.35ps

### **TMUX:**

Equation:  $Y=(AS'+BS)$

Transmission multiplexer is generally a switch that has control on the output. 2:1 MUX is designed here, where the PMOS is of size 540nm and NMOS is of size 270nm. Since the switch "S" needs an inverted function, an inverter is required. The design seems to be pretty simple and not many complications were found. The rise time with parasitic seems to be 555.9ns and fall time seems to be 734.1ns.

Rise time with parasitic: 555.9ps

Fall time with parasitic: 734.1ps

Average propagation delay: 409ps

### **Conclusion:**

Considering the design of all the combinations, the major issue was with design of metal layer, routing of the I/O ports. The design gets little complicated when the routing has to be in  $8\lambda$ ,  $8\lambda$  spacing, which is done to eliminate the violation error by router. Considering, the aspect of reducing size and the routing that take  $8\lambda$  and  $8\lambda$  area is little complicated with respect to actual design. As discussed earlier, the metal spacing issue in XOR was eliminated by routing the metal on top of PMOS. Overall, the project was very helpful in understanding the design of various CMOS logic circuits and the issues that came across gave a good experience in designing. Considering the quality, the rise time/ fall time and propagation delay gave the relationship how the output behaves with respect to input and the parasitic values. Comparing the rise time / fall time values for pre layout and post layout, there seems to be 5-10% difference due to the parasitic effects from the design on layout.

**APPENDIX:**

**DATASHEET OF INVERTER:**

Library Name:	dab8730_dab_lib	
Cell Name:	dab_INVX2	
Function/Truth Table:		
A	Y	
0	1	
1	0	
Propagation Delay:		
1. Signal A → Falling edge	247.9E-12	
Signal Y → Rising edge		
2. Signal A → Rising edge	279.5E-12	
Signal Y → Falling edge		
Output Rise Time: 310.8E-12		


Output Fall Time: 354.6E-12

Layout Area: 1.71 $\mu\text{m}$


Symbol with Port Names:



Schematic:

 

Layout:

 



### Verilog Model:

```
//Verilog HDL for "dab8730_dab_lib", "dab_INVx2" "functional"


module dab_INVx2 ( Y, A, .VDD(\VDD! ), .VSS(\VSS! ) );

    input A;
    output Y;
    input
`ifdef INCA
    (* integer inh_conn_prop_name = "VDD";
    integer inh_conn_def_value = "cds_globals.\VDD! "; *)
    \VDD! ;
    input
`ifdef INCA
    (* integer inh_conn_prop_name = "VSS";
    integer inh_conn_def_value = "cds_globals.\VSS! "; *)
    \VSS! ;

    not U1 (Y, A);

endmodule
```

### Functional Simulation Waveforms:

 

**Comments/Notes:**

Reference inverter : nMOS  $W_n/L = 270\text{nm}/45\text{nm}$

pMOS  $w_p/l = 540\text{nm}/45\text{nm}$

To maintain the equivalent resistance between pMOS and nMOS, scaling is done


After scaling: nMOS  $W_n/L = 540\text{nm}/45\text{nm}$

pMOS  $w_p/l = 1080\text{nm}/45\text{nm}$ .


$T_{pd} = 332.4\text{ps}$

**DATA SHEET FOR NAND:**


Library Name:	dab8730_dab_lib	
Cell Name:	dab_NAND2X1	
Function/Truth Table:		
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

<b>Propagation Delay:</b>	
1. Signal A → Falling edge Signal Y → Rising edge	430.8E-12
2. Signal A → Rising edge Signal Y → Falling edge	551.7E-12
3. Signal B → Falling edge Signal Y → Rising edge	431.7E-12
4. Signal B → Rising edge Signal Y → Falling edge	551.7E-12
<b>Output Rise Time: 562.2E-12</b>	
<b>Output Fall Time: 709.3E-12</b>	
<b>Layout Area: 2.052 μm</b>	
<b>Symbol with Port Names:</b>	
	

## Schematic:

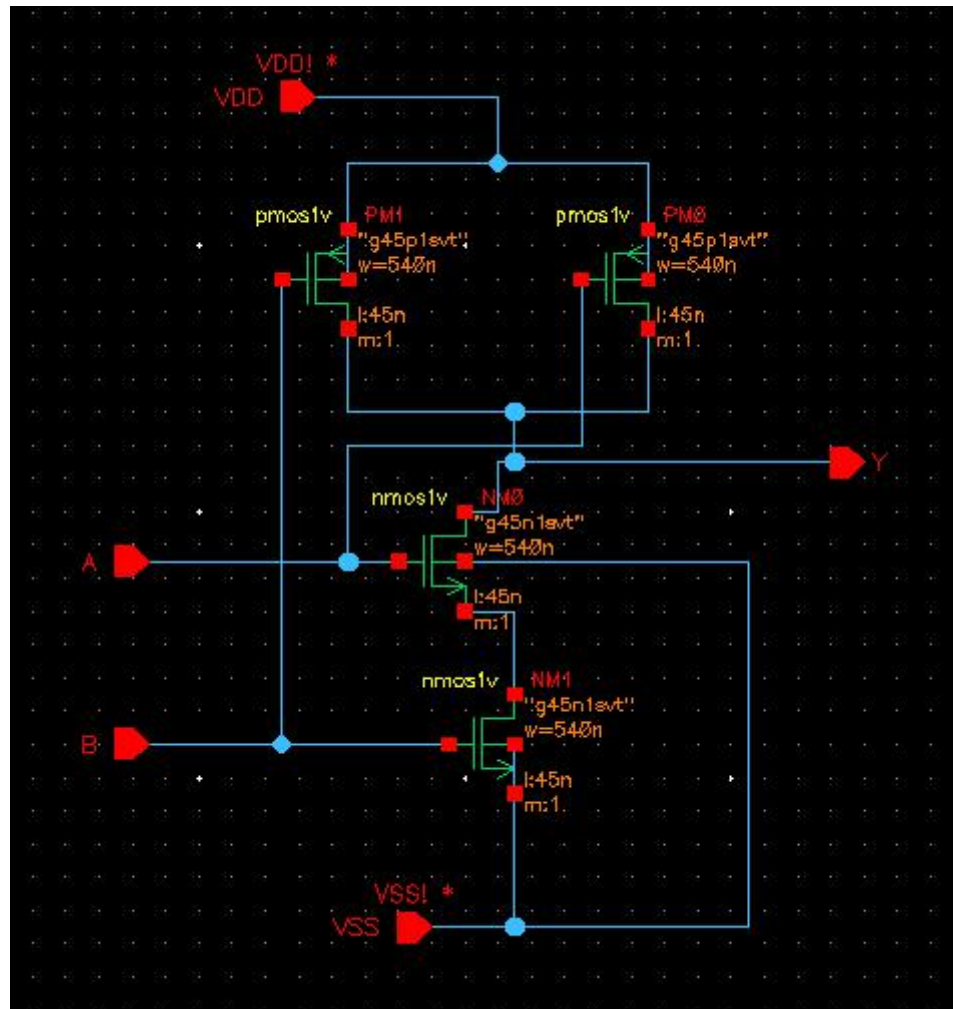

Layout:

 

## Verilog Model:

```
//Verilog HDL for "dab8730_dab_lib", "dab_NAND2X1" "functional"



module dab_NAND2X1 ( Y, A, B, .VDD(\VDD! ), .VSS(\VSS! ) );

    input A;
    output Y;
    input
`ifdef INCA
    (* integer inh_conn_prop_name = "VDD";
       integer inh_conn_def_value = "cds_globals.\VDD! "; *)
`endif
    \VDD! ;
    input
`ifdef INCA
    (* integer inh_conn_prop_name = "VSS";
       integer inh_conn_def_value = "cds_globals.\VSS! "; *)
`endif
    \VSS! ;
    input B;

    nand U1 (Y, A, B);

endmodule
```

# Functional Simulation Waveforms:

  

**Comments/Notes:**

With respect to the reference sizes, the nMOS width is doubled as they are in series with each other to maintain the equivalent resistance R across the layout.

pMOS  $W_p/L=540\text{nm}/45\text{nm}$


nMOS  $W_n/L= 540\text{nm}/45\text{nm}$

$T_{pd} = (431.7+551.7)/2 = 491.7\text{ps}$


DATA SHEET FOR NOR:

Library Name:	dab8730_dab_lib	
Cell Name:	dab_NOR2X1	
Function/Truth Table:		
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0
Propagation Delay:		




1. Signal A → Falling edge Signal Y → Rising edge	484.6E-12
2. Signal A → Rising edge Signal Y → Falling edge	548.2E-12
3. Signal B → Falling edge Signal Y → Rising edge	486.7E-12
4. Signal B → Rising edge Signal Y → Falling edge	560.1E-12
Output Rise Time: 624.1E-12	
Output Fall Time: 373.3E-12	
Layout Area: 2.5992 μm	
Symbol with Port Names:	
	

## Schematic:

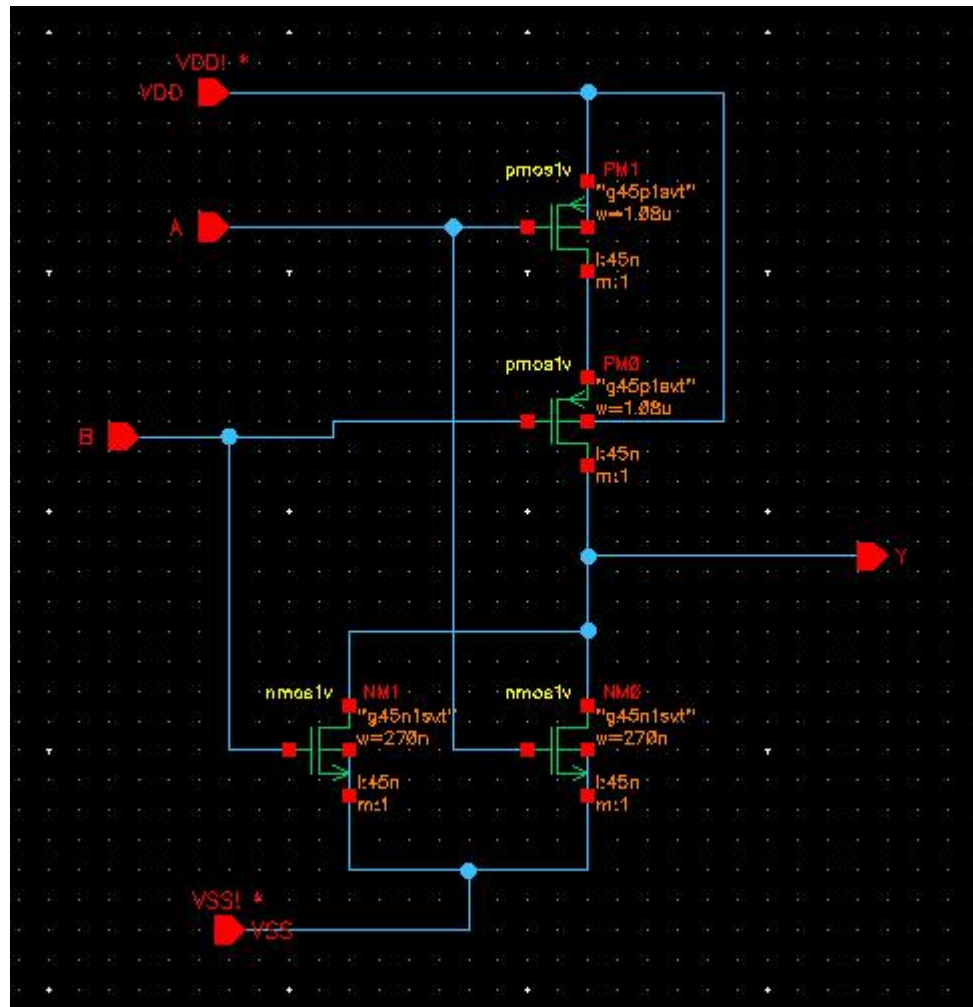

Layout:

 

## Verilog Model:

```
//Verilog HDL for "dab8730_dab_lib", "dab_NOR2X1" "functional"

module dab_NOR2X1 ( .VSS(\VSS! ), Y, A, B, .VDD(\VDD! ) );

    input A;
    output Y;
    input
`ifdef INCA
    (* integer inh_conn_prop_name = "VDD";
       integer inh_conn_def_value = "cds_globals.\VDD! "; *)
    \VDD! ;
    output
`ifdef INCA
    (* integer inh_conn_prop_name = "VSS";
       integer inh_conn_def_value = "cds_globals.\VSS! "; *)
    \VSS! ;
    input B;

    nor U1 (Y, A, B);

endmodule
```



Transient Response

Mon Sep 26 15:29:22 2016 1

Name: ...

1

V (V)

time (ns)

1

V (V)

time (ns)

1

V (V)

time (ns)

Transient Response

Mon Sep 26 15:29:22 2016 1

Name: ...

1

V (V)

time (ns)

1

V (V)

time (ns)

1

V (V)

time (ns)

Transient Response

Mon Sep 26 15:29:22 2016 1

Name: ...

1

V (V)

time (ns)

1

V (V)

time (ns)

1

V (V)


time (ns)

The figure displays three sets of circuit simulation plots, each showing the transient response of a circuit to a different input signal. Each set includes a legend, a plot of V (V) vs time (ns), and a plot of V (V) vs time (ns).

**Set 1 (Top):** The input signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is delayed by approximately 10 ns relative to the input signal.

**Set 2 (Middle):** The input signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is delayed by approximately 10 ns relative to the input signal.

 **Set 3 (Bottom):** The input signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is a square wave with a period of 100 ns, ranging from -0.1 V to 1.1 V. The output signal is delayed by approximately 10 ns relative to the input signal.



**Comments/Notes:**

With respect to the reference sizes, pMOS size is doubled to 1080nm/45nm to keep the equivalent R across the nMOS and pMOS.

pMOS  $W_p/L = 1080\text{nm}/45\text{nm}$


nMOS  $W_n/L = 270\text{nm}/45\text{nm}$

$T_{pd} = (486.7\text{ps} + 560.1\text{ps})/2 = 523.4\text{ps}$

DATA SHEET FOR OAI:


Library Name:	dab8730_dab_lib				
Cell Name:	dab_OAI22X1				
Function/Truth Table:					
A0	A1	B0	B1	Y	
0	0	0	0	1	
0	0	0	1	1	
0	0	1	0	1	
0	0	1	1	1	
0	0	0	0	1	

<b>0     1     0     1</b>	<b>0</b>
<b>0     1     1     0</b>	<b>0</b>
<b>0     1     1     1</b>	<b>0</b>
<b>1     1     0     0</b>	<b>1</b>
<b>1     0     0     1</b>	<b>0</b>
<b>1     0     1     0</b>	<b>0</b>
<b>1     0     1     1</b>	<b>0</b>
<b>1     1     0     0</b>	<b>1</b>
<b>1     1     0     1</b>	<b>0</b>
<b>1     1     1     0</b>	<b>0</b>
<b>1     1     1     1</b>	<b>0</b>
<b>Propagation Delay:</b>	
<b>1. Signal A0 -&gt; Falling</b> <b>Signal Y-&gt; Rising</b>	<b>451.9E-12</b>
<b>2. Signal A0 -&gt; Rising</b> <b>Signal Y-&gt; Falling</b>	<b>643.3E-12</b>
<b>3. Signal A1 -&gt; Falling</b> <b>Signal Y-&gt; Rising</b>	<b>449.4E-12</b>
<b>4. Signal A1 -&gt; Rising</b> <b>Signal Y-&gt;Falling</b>	<b>462.8E-12</b>

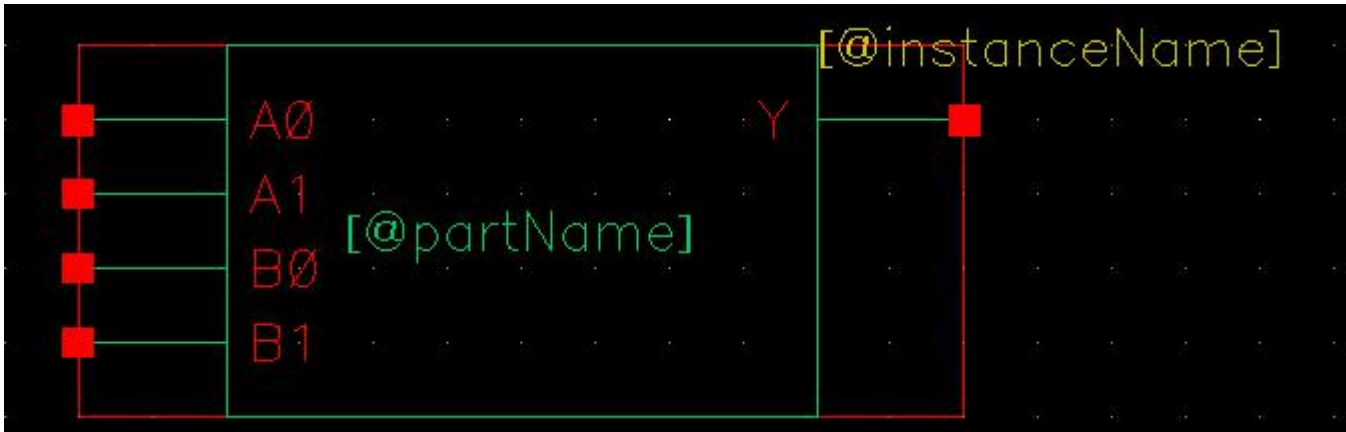
<p>5. Signal B0 -&gt; Falling</p> <p>Signal Y-&gt; Rising</p>	<p>447.9E-12</p>
<p>6. Signal B0 -&gt; Rising</p> <p>Signal Y-&gt; Falling</p>	<p>632.7E-12</p>
<p>7. Signal B1 -&gt; Falling</p> <p>Signal Y-&gt; Rising</p>	<p>450.6E-12</p>
<p>8. Signal B1 -&gt; Rising</p> <p>Signal Y-&gt;Falling</p>	<p>627.1E-12</p>
Output Rise Time: 563.6E-12	
Output Fall Time: 406.1E-12	
Layout Area: Cell Width*Cell Height = 3.1μm*1.71 μm = 5.13μm	
<p>Symbol with Port Names:</p> 	



## Schematic:

 

Layout:

 

## Verilog Model:




---

```
//Verilog HDL for "dab8730_dab_lib", "dab_OAI22X1" "functional"
```

---

```
module dab_OAI22X1 ( Y, A0, A1, B0, B1, .VDD(\VDD! ), .VSS(\VSS! ) );  
    input A0;  
    output Y;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VDD";  
       integer inh_conn_def_value = "cds_globals.\VDD! "; *)  
`endif  
    \VDD! ;  
    input B0;  
    input B1;  
    input A1;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VSS";  
       integer inh_conn_def_value = "cds_globals.\VSS! "; *)  
`endif  
    \VSS! ;  
    assign Y= ~ ((A1|B1)&(A0|B0));  
endmodule
```

## Functional Simulation Waveforms:

   

**Comments/Notes:**

The width of nMOS and pMOS are doubled with respect to the reference size as, they are in series combination the equivalent resistance across them has to be same.

pMOS  $W_p/L = 540\text{nm}/45\text{nm}$

nMOS  $W_n/L = 1080\text{nm}/45\text{nm}$

$T_{pd} = (451.9\text{ps} + 643.3\text{ns})/2 = 547.6\text{ns}$

**DATA SHEET FOR XOR:**

Library Name:	dab8730_dab_lib	
Cell Name:	dab_NOR2X1	
Function/Truth Table:		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0



**Propagation Delay:**

1. Signal A → Falling edge Signal Y → Rising edge	517E-12
2. Signal A → Rising edge Signal Y → Falling edge	547.7E-12
3. Signal B → Falling edge Signal Y → Rising edge	537.7E-12
4. Signal B → Rising edge Signal Y → Falling edge	513.4E-12

**Output Rise Time: 621.5E-12**


**Output Fall Time: 664.6E-12**

**Layout Area: 10.26  $\mu\text{m}$**


**Symbol with Port Names:**



## Schematic:

 

## Layout:

 




## Verilog Model:

```
//Verilog HDL for "dab8730_dab_lib", "dab_XOR2X1" "functional"
```

```
module dab_XOR2X1 ( Y, A, B, .VDD(\VDD! ), .VSS(\VSS! ) );  
    input A;  
    output Y;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VDD";  
       integer inh_conn_def_value = "cds_globals.\VDD! "; *)  
`endif  
    \VDD! ;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VSS";  
       integer inh_conn_def_value = "cds_globals.\VSS! "; *)  
`endif  
    \VSS! ;  
    input B;  
xor U1 (Y, A, B);  
endmodule
```



### Functional Simulation Waveforms:

   

**Comments/Notes:**

With respect to the reference size, the pMOS and nMOS are doubled to maintain the equivalent R across them. Since they are in series the resistance is  $r/2$  which increases the width over  $\times 2$ .

nMOS  $W_n/L = 540\text{nm}/45\text{nm}$

pMOS  $W_p/L = 1080\text{nm}/45\text{nm}$

$T_{pd} = (537.7\text{ps} + 547.7\text{ps}) = 542.35\text{ps}$

**DATA SHEET FOR TMUX:**


Library Name:	dab8730_dab_lib		
Cell Name:	dab_TMUX2X1		
Function/Truth Table:			
S	A	B	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

<b>Propagation Delay:</b>	
1. Signal S → Falling edge Signal Y → Rising edge	<b>372.5E-12</b>
2. Signal S → Rising edge Signal Y → Falling edge	<b>445.5E-12</b>
3. Signal A → Falling edge Signal Y → Rising edge	<b>349.09E-12</b>
4. Signal A → Rising edge Signal Y → Falling edge	<b>408.9E-12</b>
5. Signal B → Falling edge Signal Y → Rising edge	<b>347.7E-12</b>
6. Signal B → Rising edge Signal Y → Falling edge	<b>410.2E-12</b>
<b>Output Rise Time: 555.9E-12</b>	
<b>Output Fall Time: 734.1E-9</b>	
<b>Layout Area: 5.472 μm</b>	


### Symbol with Port Names:



### Schematic:

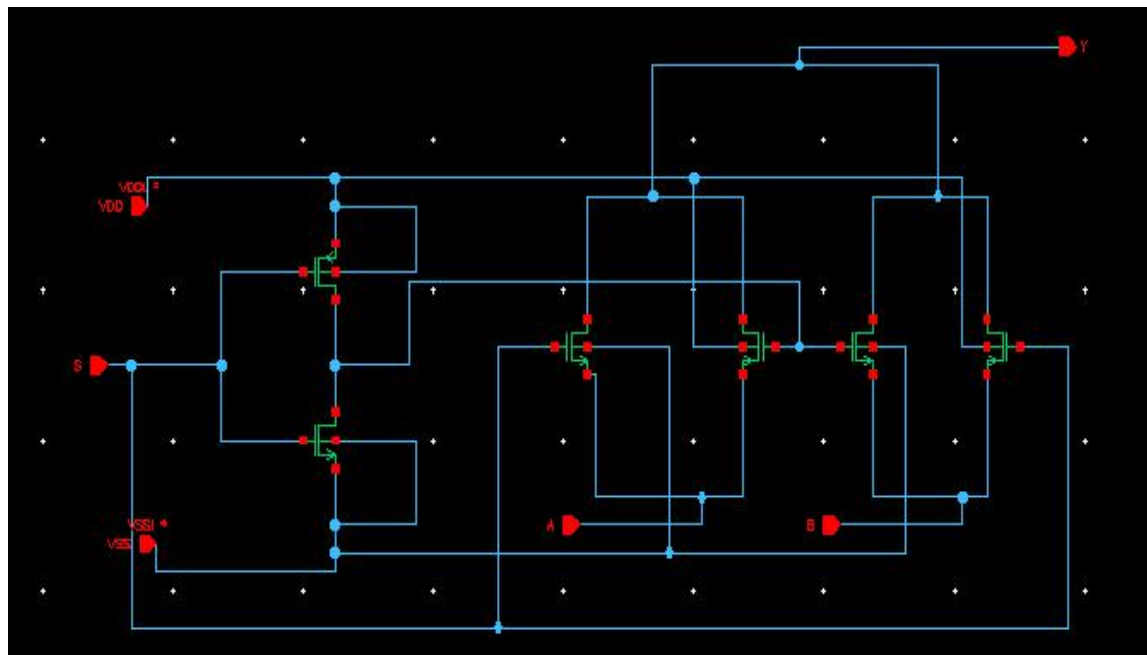

## Layout:




 


## Verilog Model:

```
//Verilog HDL for "dab8730_dab_lib", "dab_TMUX2X1" "functional"
```

```
module dab_TMUX2X1 ( Y, A, B, S, .VDD(\VDD! ), .VSS(\VSS! ) );  
  
    input A;  
    input S;  
    output Y;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VDD";  
       integer inh_conn_def_value = "cds_globals.\VDD! "; *)  
`endif  
    \VDD! ;  
    input  
`ifdef INCA  
    (* integer inh_conn_prop_name = "VSS";  
       integer inh_conn_def_value = "cds_globals.\VSS! "; *)  
`endif  
    \VSS! ;  
    input B;  
    assign Y = (((~S) & A)|(S & B));  
endmodule
```

Functional Simulation Waveforms:

    

**Comments/Notes:**

**Multiplexer acts as a unit where the output is totally controlled with respect to the signals which is fed into the switch. Multiplexer are cheap ,reduces complexity , reduces the usage of wires and also various implementation can be done.**

**pMOS  $W_p/L = 540\text{nm}/45\text{nm}$**

**nMOS  $W_n/L = 270\text{nm}/45\text{nm}$**

**$T_{pd} = (372.5\text{ps} + 445.5\text{ps})/2 = 409\text{ps}$**

